

# AC Circuits Homework 2

Daniel Halmrast

September 28, 2016

**Problem (1.a).** Consider an  $RLC$  circuit with source voltage  $V_s = V_0 \sin(\omega t)$ . Determine the current  $I = I_0 \sin(\omega t + \phi)$ .

**Solution (1.a).** Our defining differential equation is

$$V_S = \frac{1}{C}Q(t) + R\frac{dQ}{dt} + L\frac{d^2Q}{dt^2}$$

Or, in more familiar terms of  $I$ ,

$$V_S = \frac{1}{C} \int_0^t I dt + RI + L\frac{dI}{dt}$$

Substituting  $I = I_0 \sin(\omega t + \phi)$  and  $V_s = V_0 \sin(\omega t)$  we get

$$\begin{aligned} V_0 \sin(\omega t) &= \frac{1}{C} \int_0^t I_0 \sin(\omega t + \phi) dt + RI_0 \sin(\omega t + \phi) + L\frac{d}{dt}I_0 \sin(\omega t + \phi) \\ &= I_0 \left[ \frac{-1}{C\omega} \cos(\omega t + \phi) + R \sin(\omega t + \phi) + L\omega \cos(\omega t + \phi) \right] \end{aligned}$$

Using sum of angles identities, we split the RHS into  $\sin(\omega t)$  and  $\cos(\omega t)$  parts.

$$\begin{aligned} V_0 \sin(\omega t) &= \left[ I_0 R \cos(\phi) + \left( \frac{I_0}{C\omega} - I_0 L\omega \right) \sin(\phi) \right] \sin(\omega t) \\ &\quad + \left[ I_0 R \sin(\phi) + \left( I_0 L\omega - \frac{I_0}{C\omega} \right) \cos(\phi) \right] \cos(\omega t) \end{aligned}$$

Equating the coefficients yields two equations.

$$\begin{aligned} V_0 &= I_0 R \cos(\phi) + \left( \frac{I_0}{C\omega} - I_0 L\omega \right) \sin(\phi) \\ 0 &= I_0 R \sin(\phi) + \left( I_0 L\omega - \frac{I_0}{C\omega} \right) \cos(\phi) \end{aligned}$$

The second equation simplifies to

$$R \sin(\phi) = \left( \frac{1}{C\omega} - L\omega \right) \cos(\phi)$$

$$\boxed{\tan(\phi) = \frac{\frac{1}{C\omega} - L\omega}{R}} \quad (1)$$

This immediately yields the following useful identities

$$\sin(\phi) = \frac{\frac{1}{C\omega} - L\omega}{\sqrt{R^2 + \left(\frac{1}{C\omega} - L\omega\right)^2}} \quad (2)$$

$$\cos(\phi) = \frac{R}{\sqrt{R^2 + \left(\frac{1}{C\omega} - L\omega\right)^2}} \quad (3)$$

Going back to the first coefficient equality, and using results 2 and 3, we see that

$$\begin{aligned} V_0 &= I_0 R \cos(\phi) + \left( \frac{I_0}{C\omega} - I_0 L\omega \right) \sin(\phi) \\ &= I_0 \left[ R \frac{R}{\sqrt{R^2 + \left(\frac{1}{C\omega} - L\omega\right)^2}} + \left( \frac{I_0}{C\omega} - I_0 L\omega \right) \frac{\frac{1}{C\omega} - L\omega}{\sqrt{R^2 + \left(\frac{1}{C\omega} - L\omega\right)^2}} \right] \\ &= I_0 \left[ \frac{R^2 + \left(\frac{1}{C\omega} - L\omega\right)^2}{\sqrt{R^2 + \left(\frac{1}{C\omega} - L\omega\right)^2}} \right] \\ &= I_0 \sqrt{R^2 + \left(\frac{1}{C\omega} - L\omega\right)^2} \end{aligned}$$

Therefore

$$\boxed{I_0 = \frac{V_0}{\left(R^2 + \left(\frac{1}{C\omega} - L\omega\right)^2\right)^{\frac{1}{2}}}} \quad (4)$$

**Problem (1.d).** *Solve for the voltage across the capacitor, using  $V_C = \frac{Q(t)}{C}$*