

AC Circuits Homework 2

Daniel Halmrast

September 28, 2016

Problem 1 (1.a). *Consider an RLC circuit with source voltage $V_s = V_0 \sin(\omega t)$. Determine the current $I = I_0 \sin(\omega t + \phi)$.*

Solution 1 (1.a). Our defining differential equation is

$$V_s = \frac{1}{C}Q(t) + R\frac{dQ}{dt} + L\frac{d^2Q}{dt^2}$$