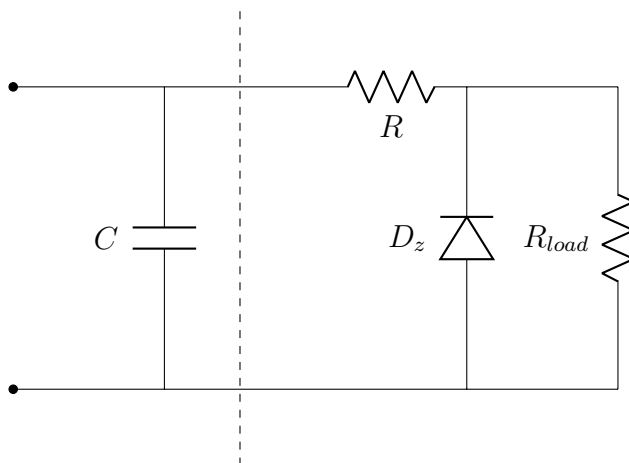


# Power Supply Homework 2: The Zener Diode

Daniel Halmrast

October 6, 2016

Using The parameters  $V_{out}, i_{load}, \langle P_z \rangle, I_{zmin}, V_p, f$ , solve for the parameters  $R, C, \Delta V$  in the following circuit.



Firstly, we concern ourselves with the ripple voltage. We know from earlier analysis that the ripple voltage is given as

$$\Delta V = V_p \frac{1}{C R_{eq} f}$$

It is clear from analysis of the right side that the Thevenin equivalent resistance is just  $R$ . Thus, we have

$$\boxed{\Delta V = V_p \frac{1}{C R f}} \quad (1)$$

Next, we will analyze the average power requirement. It can be approximated that the average power through the Zener diode is

$$\langle P_z \rangle = \overline{IV}$$

Thus,

$$\begin{aligned}\bar{I} &= \frac{\langle P_z \rangle}{V_{out}} \\ i_{zmax} - \frac{\Delta i_z}{2} &= \frac{\langle P_z \rangle}{V_{out}}\end{aligned}$$

Since  $i_z = i_R - i_l$ , and  $i_R = \frac{v_r}{R}$ , it follows that

$$\begin{aligned}\frac{V_p - V_{out}}{R} - i_l - \frac{\Delta i_z}{2} &= \frac{\langle P_z \rangle}{V_{out}} \\ \frac{V_p - V_{out}}{R} - i_l - \frac{\Delta V}{2R} &= \frac{\langle P_z \rangle}{V_{out}} \\ V_p - V_{out} - i_l R - \frac{\Delta V}{2} &= \frac{\langle P_z \rangle}{V_{out}} R\end{aligned}$$

Thus,

$$\boxed{V_p - V_{out} - \frac{\Delta V}{2} = \left( \frac{\langle P_z \rangle}{V_{out}} - i_l \right) R} \quad (2)$$

Finally, we will analyze the minimum current requirement. Following a similar process to equation (2),

$$\begin{aligned}i_{zmin} &= i_{zmax} - \Delta i \\ &= i_{Rmax} - i_l - \Delta i \\ &= \frac{V_p - V_{out}}{R} - i_l - \frac{\Delta V}{R} \\ i_{zmin} R &= V_p - V_{out} - i_l R - \Delta V\end{aligned}$$

This leads to the final relation

$$\boxed{V_p - V_{out} - \Delta V = (i_{zmin} + i_l) R} \quad (3)$$