

AC Circuits Homework 2

Daniel Halmrast

September 28, 2016

Problem 1. *1.a Consider an RLC circuit with source voltage $V_s = V_0 \sin(\omega t)$. Determine the current $I = I_0 \sin(\omega t + \phi)$.*